

國立台灣科技大學九十七學年度碩士班招生試題

系所組別： 電機工程系碩士班丁組
 科目： 邏輯設計

本試題總分: 100

Problem #1 (18%)

- (a) Give the 6-bit sign-magnitude, 1's complement, and 2's complement representations for decimal 3 and -7.
 (b) Convert decimal 51768 into hexadecimal, octal, and binary.

Problem #2 (12%)

- (a) Given $f(a, b, c, d) = \sum m(0, 2, 5, 7, 8, 10, 13, 15)$. Find the minimum POS and SOP expressions by using a Karnaugh map.
 (b) Given $f(a, b, c, d, e) = \sum m(0, 1, 6, 10, 12, 14, 16, 17, 26, 30)$. Find the minimum SOP expression using a 5-variable K-map.

Problem #3 (10%)

- (a) Use NOR gates to draw the circuit for the function $F = abc' + ab'c' + a'bc$
 (b) Use NAND gates to implement $f_{abc} = \prod M(0, 3, 5, 7)$.

Problem #4 (10%)

Realize $f(a, b, c) = \sum m(2, 4, 5, 7)$ with a 4-to-1 multiplexer module.

Problem #5 (10%)

A PN flip-flop has four operations, clear to 0, no change, complement, and set to 1, when inputs P and N are 00, 01, 10, and 11, respectively.

- (a) Show the characteristic table.
 (b) Show the characteristic equation.

Problem #6 (10%)

A sequential circuit has two JK flip-flops A and B and one input x. The circuit is described by the following flip-flop input equations:

$$J_A = B, K_A = Bx'$$

$$J_B = x', K_B = A'x + Ax'$$

- (a) Derive the state equations $A(t+1)$ and $B(t+1)$ by substituting the input equations for the J and K variables.
 (b) Draw the state diagram of the circuit.

Problem #7 (10%)

Draw the logic diagram of a four-bit register with four D flip-flops and four 4*1 multiplexers with mode selection inputs S_1 and S_0 . The register operates according to the following function table:

S_1	S_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load



國立台灣科技大學九十七學年度碩士班招生試題

系所組別： 電機工程系碩士班丁組

科 目： 邏輯設計

Problem #8 (20%)

It is necessary to formulate the Hamming code for four data bits, D_3 , D_5 , D_6 and D_7 , together with three parity bits, P_1 , P_2 and P_4 .

(a) Evaluate the 7-bit composite code word for the data word 0010.

(b) Evaluate three check bits, C_4 , C_2 and C_1 , assuming no error.

(c) Assume an error in bit D_5 during writing into memory. Show how the error in the bit is detected and corrected.

(d) Add parity bit P_8 to include double-error detection in the code. Assume that error occurred in bit P_2 and D_5 . Show how the double error is detected.

